

4.
$$H(s) = \frac{V_o(s)}{V_g(s)} = \frac{b}{s^2 + \omega s + b}$$

$$\alpha = \frac{\alpha}{2} \qquad \beta = \sqrt{b - \left(\frac{\alpha}{2}\right)^2} \qquad \Rightarrow \qquad \beta^2 = b - \left(\frac{\alpha}{2}\right)^2 \Rightarrow \qquad b = \alpha^2 + \beta^2$$

$$\alpha = 2 \alpha \qquad \qquad \beta^2 = b - \frac{4\alpha^2}{4} \qquad \Rightarrow \qquad b = \alpha^2 + \beta^2$$

$$R_4 = R_5 = 1 \text{ k} \Omega \qquad C_1 = C_2 = 0.1 \text{ MF}$$

$$R_4 = R_5 = 1 \text{ k.}\Omega$$
 $C_1 = C_2 = 0.1 \text{ NF}$

$$R_1 = R_2 = \frac{2}{9}10^7$$

$$R_3 = \frac{9}{5}10^7$$

$$H(s) \cdot V_{g(s)} = V_{o}(s)$$
 $V_{o}(s) = \frac{1}{s} \left[\frac{b}{s^2 + as + b} \right]$

$$V_{g}(s) = \frac{1}{s}$$


$$V_{o}(s) = \frac{\alpha^{2} + \beta^{2}}{s[s^{2} + 2\alpha s + \alpha^{2} + \beta^{2}]} = \frac{\alpha^{2} + \beta^{2}}{s[(s + \alpha)^{2} + \beta^{2}]}$$


$$\frac{A}{5} + \frac{B_{5} + C}{(5 + \infty)^{2} + B^{2}} < \frac{A}{5} \cdot \frac{\alpha x^{2} + B^{2}}{\alpha x^{2} + B^{2}} = 1$$


$$5^{2} (B + 1) = 0 \qquad s(C + 2\infty) = 0$$

$$=\frac{1}{5}-\frac{\left(5+2\alpha\right)}{\left(5+\alpha\xi\right)+\beta^{2}}=\frac{1}{5}-\frac{\left(5+\alpha\xi\right)+\alpha\xi}{\left(5+\alpha\xi\right)+\beta^{2}}=\frac{1}{5}-\frac{\left(5+\alpha\xi\right)}{\left(5+\alpha\xi\right)+\beta^{2}}+\frac{\alpha\xi}{\left(5+\alpha\xi\right)^{2}+\beta^{2}}$$

Circuit 1:

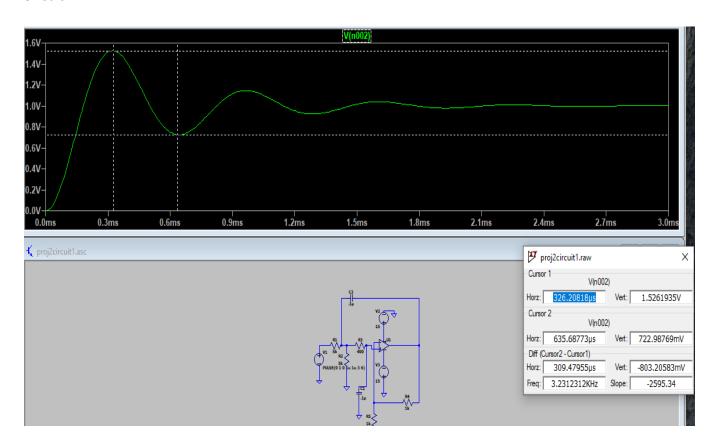

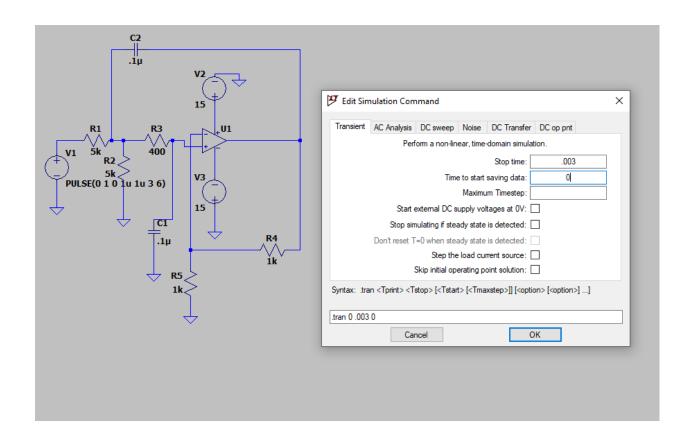

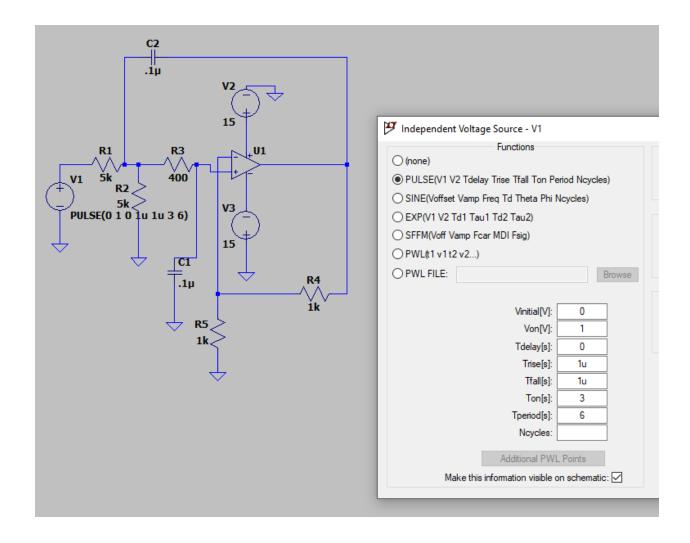

Circuit 2:

