
Table of Contents

ELEN 100L (Electric Circuits II): Project 2, Christian Garcia Alexander Luo	1
Setup global variables	1
Problem 2	2
Problem 3	5
Problem 6	7
Program execution complete	11
MATLAB code listing	11

ELEN 100L (Electric Circuits II): Project 2, Christian Garcia Alexander Luo

```
clear; clc; clf; cla; close all;  
format long; format compact;
```

Setup global variables

```
% These Ideal Design element values are fixed in the circuit.  
VG = 1 ; % Generator voltage  
  
Vdd_pos = 15 ; % Positive power supply voltage  
Vdd_neg = -15 ; % Negative power supply voltage  
  
R1_ideal_2 = 5000 ; % Ohms  
R2_ideal_2 = 5000 ; % Ohms  
R3_ideal_2 = 400 ; % Ohms  
R4_ideal_2 = 1000 ; % Ohms  
R5_ideal_2 = 1000 ; % Ohms  
C1_ideal_2 = 0.1e-6 ; % Farads  
C2_ideal_2 = 0.1e-6 ; % Farads  
  
R1_ideal_6 = 1000 ; % Ohms  
R2_ideal_6 = 1000 ; % Ohms  
R3_ideal_6 = 740.938 ; % Ohms  
R4_ideal_6 = 1000 ; % Ohms  
R5_ideal_6 = 1000 ; % Ohms  
C1_ideal_6 = 0.1e-6 ; % Farads  
C2_ideal_6 = 0.1e-6 ; % Farads  
  
% Build an array for the R elements.  
R_ideal_2 = [R1_ideal_2, R2_ideal_2, R3_ideal_2, R4_ideal_2,  
R5_ideal_2];  
R_ideal_6 = [R1_ideal_6, R2_ideal_6, R3_ideal_6, R4_ideal_6,  
R5_ideal_6];  
  
% Build an array for the C elements.  
C_ideal_2 = [ (0), (0), (0), (0), (0)  
; ...
```

```

        (0), -(C1_ideal_2),          (0), (0),
(C1_ideal_2); ...
        (0),          (0), -(C2_ideal_2), (0), (0)
; ...
        (0),          (0),          (0), (0), (0)
; ...
        (0),          (0),          (0), (0), (0)          ];

C_ideal_6 = [ (0),          (0),          (0), (0), (0)
; ...
        (0), -(C1_ideal_6),          (0), (0),
(C1_ideal_6); ...
        (0),          (0), -(C2_ideal_6), (0), (0)
; ...
        (0),          (0),          (0), (0), (0)
; ...
        (0),          (0),          (0), (0), (0)          ];

% Build an array for the source elements.
B = [ VG; 0; 0; 0; 0 ];

% Build an array for the the time vector.
time2 = [0, 3*10^(-3)];
time6 = [0, 1*10^(-3)];

% Build an array for the the initial conditions.
x0 = [0; 0; 0; 0; 0];      % Assume everything is zero to start

% These values are used for plotting purposes.
fignum = 1;

plot_left_2   = 0;   plot_right_2 = time2(2);   % x-axis range
(seconds)
plot_bottom_2 = 0;   plot_top_2   = VG+0.6;      % y-axis range (volts)

plot_left_6   = 0;   plot_right_6 = time6(2);   % x-axis range
(seconds)
plot_bottom_6 = 0;   plot_top_6   = VG+0.2;      % y-axis range (volts)

```

Problem 2

```

% Display the component values for the Ideal design.
%

disp(' ');
disp('The Ideal Design component values are:');
fprintf('    R1 = %+11.4f Ohms.\n', R1_ideal_2 );
fprintf('    R2 = %+11.4f Ohms.\n', R2_ideal_2 );
fprintf('    R3 = %+11.4f Ohms.\n', R3_ideal_2 );
fprintf('    R4 = %+11.4f Ohms.\n', R4_ideal_2 );
fprintf('    R5 = %+11.4f Ohms.\n', R5_ideal_2 );
fprintf('    C1 = %+11.4e Farads.\n', C1_ideal_2 );

```

```
fprintf('      C2 = %+11.4e Farads.\n', C2_ideal_2 );
```

The Ideal Design component values are:

```
R1 = +5000.0000 Ohms.  
R2 = +5000.0000 Ohms.  
R3 = +400.0000 Ohms.  
R4 = +1000.0000 Ohms.  
R5 = +1000.0000 Ohms.  
C1 = +1.0000e-07 Farads.  
C2 = +1.0000e-07 Farads.
```

Calculate the MATLAB transient response for the Ideal design.

```
% Update the resistor variables used in the proj2E100_transient  
function  
% before calling the ode23t solver.  
R1_circuit = R1_ideal_2;  
R2_circuit = R2_ideal_2 ;  
R3_circuit = R3_ideal_2 ;  
R4_circuit = R4_ideal_2 ;  
R5_circuit = R5_ideal_2 ;  
  
options = odeset('mass', C_ideal_2 , 'RelTol', 0.1e-9);  
[t2, x2] = ode23t( @proj2E100_transient , [0 5] , x0 , options );  
  
% Capture peak overshoot and undershoot voltages with indexes.  
[v5_pk_overshoot_ideal_2 , ...  
  v5_pk_overshoot_ideal_index_2 ] = max( x2(:,5) );  
[v5_pk_undershoot_ideal_2 , ...  
  v5_pk_undershoot_ideal_index_2] = ...  
  min( x2(v5_pk_overshoot_ideal_index_2 + 1:size(t2),5) );  
v5_pk_undershoot_ideal_index_2 = ...  
  v5_pk_undershoot_ideal_index_2 + v5_pk_overshoot_ideal_index_2;  
  
% Capture peak overshoot and undershoot time stamps at peak indexes.  
t2_pk_overshoot_ideal_2 = t2( v5_pk_overshoot_ideal_index_2);  
t2_pk_undershoot_ideal_2 = t2(v5_pk_undershoot_ideal_index_2);  
  
Generate the MATLAB plot for the transient response.  
  
fignum = fignum+1; figObj = figure(fignum); % Establish a figure  
number  
set(fignum, 'Name', ...  
  ['Prob 2: Transient Response Ideal Design']); % Name the figure  
  
Tr_ideal_2_Plot = plot(t2, x2); % Generate plot  
grid on; % Turn grid on  
xlabel('Time (seconds)'); % Label the x-axis  
ylabel('Amplitude (volts)'); % Label the y-axis  
axis([plot_left_2, plot_right_2, ...  
  plot_bottom_2, plot_top_2]); % Bound plot  
title(['Figure ', num2str(fignum, '%-2.u'), ...  
  ': Problem 2 Transient Response Ideal Design']);  
legend('v_1(t)', 'v_2(t)', 'v_3(t)', 'v_4(t)', 'v_5(t)', ...
```


```

'Location', 'NorthEast');

% Add annotation to the plot.
strmax = ['\leftarrow ', num2str(t2_pk_overshoot_ideal_2 * 1e6), ...
          '\mu s, ', num2str(v5_pk_overshoot_ideal_2), 'V'];
text(t2_pk_overshoot_ideal_2, ...
     v5_pk_overshoot_ideal_2, ...
     strmax, 'HorizontalAlignment', 'left', 'FontWeight', 'bold');

strmin = ['\leftarrow ', num2str(t2_pk_undershoot_ideal_2 * 1e6), ...
          '\mu s, ', num2str(v5_pk_undershoot_ideal_2), 'V'];
text(t2_pk_undershoot_ideal_2, ...
     v5_pk_undershoot_ideal_2, ...
     strmin, 'HorizontalAlignment', 'left', 'FontWeight', 'bold');

```

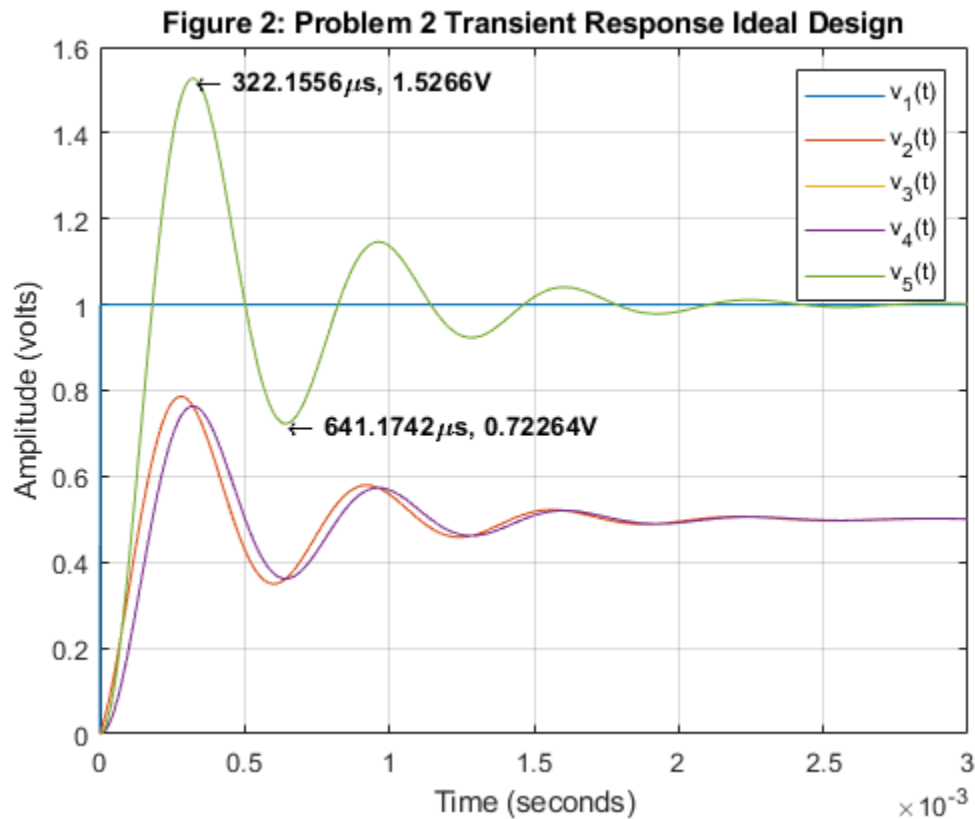

Display the MATLAB peak overshoot and undershoot values for the Ideal design.

```

disp(' ');
disp('The MATLAB peak overshoot and undershoot values are:');
fprintf('      V5 p.o. = %+11.4f Volts.\n', v5_pk_overshoot_ideal_2);
fprintf('      V5 p.u. = %+11.4f Volts.\n',
        v5_pk_undershoot_ideal_2 );
fprintf('      t p.o. = %+11.4e seconds.\n', t2_pk_overshoot_ideal_2 );
fprintf('      t p.u. = %+11.4e seconds.\n',
        t2_pk_undershoot_ideal_2 );

```

The MATLAB peak overshoot and undershoot values are:

```
V5 p.o. =      +1.5266 Volts.  
V5 p.u. =      +0.7226 Volts.  
t p.o. = +3.2216e-04 seconds.  
t p.u. = +6.4117e-04 seconds.
```

Problem 3

```
%This part requires screenshots for:  
% LTSpice schematic  
% The LTSpice voltage source setup (this is the gray settings box)  
% The LT model transient analysis simulation setup(simulation  
  settings)  
% The LTSpice simulation result  
  
% Capture peak overshoot and undershoot voltages from the LTSpice  
  plot.  
ltspice_v5_pk_overshoot_ideal_2 = 1.527 ;  
ltspice_v5_pk_undershoot_ideal_2 = 0.722 ;  
  
% Capture peak overshoot and undershoot time stamps from the LTSpice  
  plot.  
ltspice_t2_pk_overshoot_ideal_2 = 0.000317848 ;  
ltspice_t2_pk_undershoot_ideal_2 = 0.00063569 ;
```

Display the LTSpice peak overshoot and undershoot values for the Ideal design.

```
disp(' ');  
disp('The LTSpice peak overshoot and undershoot values are:');  
fprintf('      V5 p.o. = %+11.4f Volts.\n', ...  
    ltspice_v5_pk_overshoot_ideal_2);  
fprintf('      V5 p.u. = %+11.4f Volts.\n', ...  
    ltspice_v5_pk_undershoot_ideal_2);  
fprintf('      t p.o. = %+11.4e seconds.\n', ...  
    ltspice_t2_pk_overshoot_ideal_2);  
fprintf('      t p.u. = %+11.4e seconds.\n', ...  
    ltspice_t2_pk_undershoot_ideal_2);
```

The LTSpice peak overshoot and undershoot values are:

```
V5 p.o. =      +1.5270 Volts.  
V5 p.u. =      +0.7220 Volts.  
t p.o. = +3.1785e-04 seconds.  
t p.u. = +6.3569e-04 seconds.
```

Calculate the percent difference at the peak overshoot and undershoot values between MATLAB and LTSpice Ideal Designs.

```
diff_ideal_v5_pk_overshoot_2 = ...  
    (ltspice_v5_pk_overshoot_ideal_2 - v5_pk_overshoot_ideal_2) ...  
    /abs(v5_pk_overshoot_ideal_2)*100;  
diff_ideal_v5_pk_undershoot_2 = (ltspice_v5_pk_undershoot_ideal_2 -  
    v5_pk_undershoot_ideal_2) ...
```

```

    /abs(v5_pk_undershoot_ideal_2)*100 ;

diff_ideal_t2_pk_overshoot_2 = (ltspice_t2_pk_overshoot_ideal_2 -
    t2_pk_overshoot_ideal_2) ...
    /abs(t2_pk_overshoot_ideal_2)*100 ;
diff_ideal_t2_pk_undershoot_2 = (ltspice_t2_pk_undershoot_ideal_2 -
    t2_pk_undershoot_ideal_2) ...
    /abs(t2_pk_undershoot_ideal_2)*100 ;

disp(' ');
disp('The % difference between MATLAB and LTSpice at the peaks:');
fprintf('    MATLAB V5 p.o. = %+11.4f Volts.\n', ...
    v5_pk_overshoot_ideal_2);
fprintf('    LTSpice V5 p.o. = %+11.4f Volts.\n', ...
    ltspice_v5_pk_overshoot_ideal_2);
fprintf('    %% diff = %+8.4f (%%).\n', ...
    diff_ideal_v5_pk_overshoot_2);

fprintf('    MATLAB V5 p.u. = %+11.4f Volts.\n',
    v5_pk_undershoot_ideal_2 );
fprintf('    LTSpice V5 p.u. = %+11.4f Volts.\n',
    ltspice_v5_pk_undershoot_ideal_2 );
fprintf('    %% diff = %+8.4f (%%).\n',
    diff_ideal_v5_pk_undershoot_2 );

fprintf('    MATLAB t p.o. = %+11.4e seconds.\n',
    t2_pk_overshoot_ideal_2 );
fprintf('    LTSpice t p.o. = %+11.4e seconds.\n',
    ltspice_t2_pk_overshoot_ideal_2 );
fprintf('    %% diff = %+8.4f (%%).\n',
    diff_ideal_t2_pk_overshoot_2 );
fprintf('    MATLAB t p.u. = %+11.4e seconds.\n',
    t2_pk_undershoot_ideal_2 );
fprintf('    LTSpice t p.u. = %+11.4e seconds.\n',
    ltspice_t2_pk_undershoot_ideal_2 );
fprintf('    %% diff = %+8.4f (%%).\n',
    diff_ideal_t2_pk_undershoot_2 );

```

The % difference between MATLAB and LTSpice at the peaks:

```

MATLAB V5 p.o. =    +1.5266 Volts.
LTSpice V5 p.o. =    +1.5270 Volts.
% diff =  +0.0247 (%).
MATLAB V5 p.u. =    +0.7226 Volts.
LTSpice V5 p.u. =    +0.7220 Volts.
% diff =  -0.0881 (%).
MATLAB t p.o. = +3.2216e-04 seconds.
LTSpice t p.o. = +3.1785e-04 seconds.
% diff =  -1.3371 (%).
MATLAB t p.u. = +6.4117e-04 seconds.
LTSpice t p.u. = +6.3569e-04 seconds.
% diff =  -0.8553 (%).

```

Problem 6

Display the component values for the Ideal design.

```
disp(' ');
disp('The Ideal Design component values are:');
fprintf('    R1 = %+11.4f Ohms.\n', R1_ideal_6 );
fprintf('    R2 = %+11.4f Ohms.\n', R2_ideal_6 );
fprintf('    R3 = %+11.4f Ohms.\n', R3_ideal_6 );
fprintf('    R4 = %+11.4f Ohms.\n', R4_ideal_6 );
fprintf('    R5 = %+11.4f Ohms.\n', R5_ideal_6 );
fprintf('    C1 = %+11.4e Farads.\n', C1_ideal_6 );
fprintf('    C2 = %+11.4e Farads.\n', C2_ideal_6 );
```

The Ideal Design component values are:

```
R1 = +1000.0000 Ohms.
R2 = +1000.0000 Ohms.
R3 = +740.9380 Ohms.
R4 = +1000.0000 Ohms.
R5 = +1000.0000 Ohms.
C1 = +1.0000e-07 Farads.
C2 = +1.0000e-07 Farads.
```

Calculate the MATLAB transient response for the Ideal design.

```
% Update the resistor variables used in the proj2E100_transient
function
% before calling the ode23t solver.
R1_circuit = R1_ideal_6;
R2_circuit = R2_ideal_6 ;
R3_circuit = R3_ideal_6 ;
R4_circuit = R4_ideal_6 ;
R5_circuit = R5_ideal_6 ;

%ODE solution, refer to the example in Problem 2
options = odeset('mass', C_ideal_6 , 'RelTol', 0.1e-9);
[t6, x6] = ode23t( @proj2E100_transient, [0 5] , x0 , options );

% Capture peak overshoot and undershoot voltages with indexes.
[v5_pk_overshoot_ideal_6 , ...
  v5_pk_overshoot_ideal_index_6 ] = max( x6(:,5) );
[v5_pk_undershoot_ideal_6, ...
  v5_pk_undershoot_ideal_index_6] = ...
  min( x6(v5_pk_overshoot_ideal_index_6 + 1:size(t6),5) );
v5_pk_undershoot_ideal_index_6 = ...
  v5_pk_undershoot_ideal_index_6 + v5_pk_overshoot_ideal_index_6;

% Capture peak overshoot and undershoot time stamps at peak indexes.
t6_pk_overshoot_ideal_6 = t6( v5_pk_overshoot_ideal_index_6 );
t6_pk_undershoot_ideal_6 = t6(v5_pk_undershoot_ideal_index_6);
```

Generate the MATLAB plot for the transient response.

```


fignum = fignum+1; figObj = figure(fignum); % Establish a figure
number
set(fignum, 'Name', ...
    ['Prob 6: Transient Response Ideal Design']); % Name the figure

Tr_ideal_6_Plot = plot( t6 , x6 ); % Generate plot
grid on; % Turn grid on
xlabel('Time (seconds)'); % Label the x-axis
ylabel('Amplitude (volts)'); % Label the y-axis
axis([plot_left_6, plot_right_6, ...
    plot_bottom_6, plot_top_6]); % Bound plot
title(['Figure ', num2str(fignum, '%-2.u'), ...
    ': Problem 6 Transient Response Ideal Design']);
legend('v_1(t)', 'v_2(t)', 'v_3(t)', 'v_4(t)', 'v_5(t)', ...
    'Location', 'NorthEast');

% Add annotation to the plot.
strmax = ['\leftarrow ', num2str(t6_pk_overshoot_ideal_6 * 1e6), ...
    '\mus, ', num2str(v5_pk_overshoot_ideal_6), 'V'];
text(t6_pk_overshoot_ideal_6, ...
    v5_pk_overshoot_ideal_6, ...
    strmax, 'HorizontalAlignment', 'left', 'FontWeight', 'bold');

strmin = [num2str(t6_pk_undershoot_ideal_6 * 1e6), ...
    '\mus, ', num2str(v5_pk_undershoot_ideal_6), 'V
    \rightarrow'];
text(t6_pk_undershoot_ideal_6, ...
    v5_pk_undershoot_ideal_6, ...
    strmin, 'HorizontalAlignment', 'right', 'FontWeight', 'bold');

```

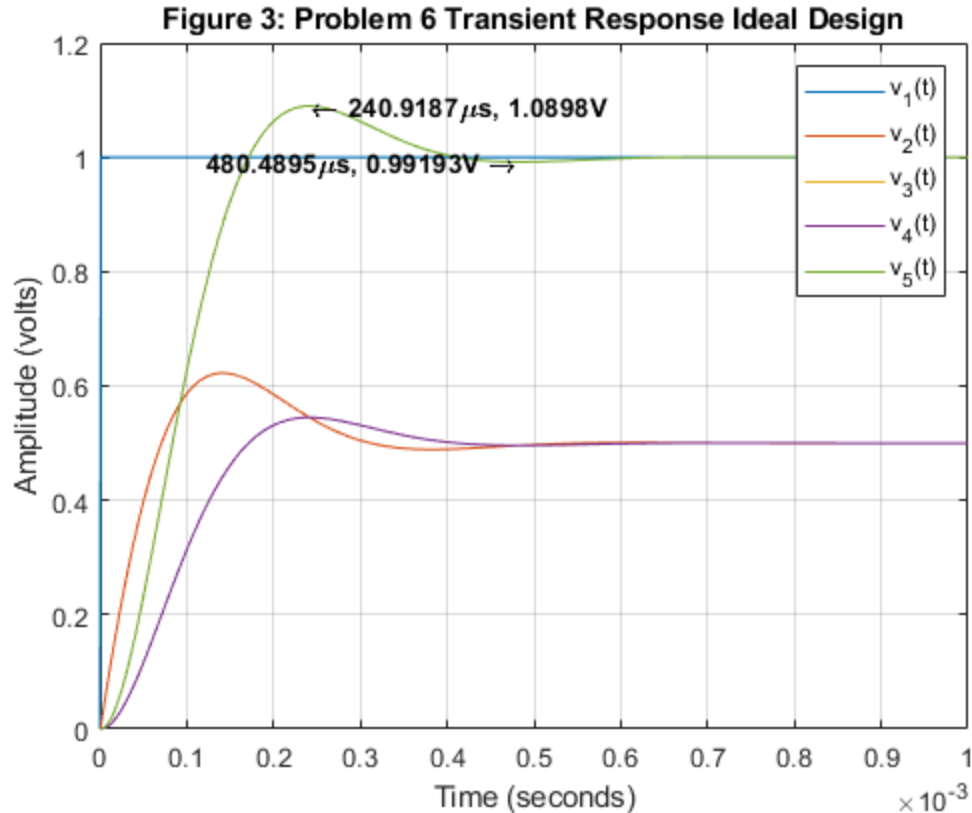

Display the MATLAB peak overshoot and undershoot values for the Ideal design.

```
disp(' ');
disp('The MATLAB peak overshoot and undershoot values are:');
fprintf('    V5 p.o. = %+11.4f Volts.\n', v5_pk_overshoot_ideal_6);
fprintf('    V5 p.u. = %+11.4f Volts.\n', v5_pk_undershoot_ideal_6);
fprintf('    t p.o. = %+11.4e seconds.\n', t6_pk_overshoot_ideal_6);
fprintf('    t p.u. = %+11.4e seconds.\n', t6_pk_undershoot_ideal_6);
```

The MATLAB peak overshoot and undershoot values are:

```
V5 p.o. =    +1.0898 Volts.
V5 p.u. =    +0.9919 Volts.
t p.o. = +2.4092e-04 seconds.
t p.u. = +4.8049e-04 seconds.
```

%This part requires screenshots of:

```
% The LTSpice schematic for the circuit
% The LTSpice voltage source setup for the circuit
% The LTSpice model transient analysis simulation setup %%
% The LTSpice simulation result is shown below.
```

% Capture peak overshoot and undershoot voltages from the plot.

```
ltspice_v5_pk_overshoot_ideal_6 = 1.09 ;
ltspice_v5_pk_undershoot_ideal_6 = 0.9918 ;
```

% Capture peak overshoot and undershoot time stamps from the plot.

```
ltspice_t6_pk_overshoot_ideal_6 = 0.00023978 ;
ltspice_t6_pk_undershoot_ideal_6 = 0.000479554 ;
```

Display the LTSpice peak overshoot and undershoot values for the Ideal design.

```
disp(' ');
disp('The LTSpice peak overshoot and undershoot values are:');
fprintf('    V5 p.o. = %+11.4f Volts.\n', v5_pk_overshoot_ideal_6 );
fprintf('    V5 p.u. = %+11.4f Volts.\n', v5_pk_undershoot_ideal_6);
fprintf('    t p.o. = %+11.4e seconds.\n', t6_pk_overshoot_ideal_6 );
fprintf('    t p.u. = %+11.4e seconds.\n',
    t6_pk_undershoot_ideal_6 );
```

The LTSpice peak overshoot and undershoot values are:

```
V5 p.o. =      +1.0898 Volts.
V5 p.u. =      +0.9919 Volts.
t p.o. = +2.4092e-04 seconds.
t p.u. = +4.8049e-04 seconds.
```

Calculate the percent difference at the peak overshoot and undershoot values between MATLAB and LTSpice Ideal Designs.

```
diff_ideal_v5_pk_overshoot_6 = ...
    (ltspice_v5_pk_overshoot_ideal_6 - v5_pk_overshoot_ideal_6) ...
    /abs(v5_pk_overshoot_ideal_6)*100;
diff_ideal_v5_pk_undershoot_6 = ...
    (ltspice_v5_pk_undershoot_ideal_6 - v5_pk_undershoot_ideal_6) ...
    /abs(v5_pk_undershoot_ideal_6)*100;

diff_ideal_t6_pk_overshoot_6 = ...
    (ltspice_t6_pk_overshoot_ideal_6 - t6_pk_overshoot_ideal_6) ...
    /abs(t6_pk_overshoot_ideal_6)*100;
diff_ideal_t6_pk_undershoot_6 = ...
    (ltspice_t6_pk_undershoot_ideal_6 - t6_pk_undershoot_ideal_6) ...
    /abs(t6_pk_undershoot_ideal_6)*100;

disp(' ');
disp('The % difference between MATLAB and LTSpice at the peaks:');
fprintf('    MATLAB V5 p.o. = %+11.4f Volts.\n', ...
    v5_pk_overshoot_ideal_6);
fprintf('    LTSpice V5 p.o. = %+11.4f Volts.\n', ...
    ltspice_v5_pk_overshoot_ideal_6);
fprintf('    %% diff = %+8.4f (%%).\n', ...
    diff_ideal_v5_pk_overshoot_6);
fprintf('    MATLAB V5 p.u. = %+11.4f Volts.\n', ...
    v5_pk_undershoot_ideal_6);
fprintf('    LTSpice V5 p.u. = %+11.4f Volts.\n', ...
    ltspice_v5_pk_undershoot_ideal_6);
fprintf('    %% diff = %+8.4f (%%).\n', ...
    diff_ideal_v5_pk_undershoot_6);

fprintf('    MATLAB t p.o. = %+11.4e seconds.\n', ...
    t6_pk_overshoot_ideal_6);
fprintf('    LTSpice t p.o. = %+11.4e seconds.\n', ...
```

```

        ltspice_t6_pk_overshoot_ideal_6);
fprintf('        %% diff = %+8.4f (%%).\n', ...
        diff_ideal_t6_pk_overshoot_6);
fprintf('        MATLAB    t p.u. = %+11.4e seconds.\n', ...
        t6_pk_undershoot_ideal_6);
fprintf('        LTSpice    t p.u. = %+11.4e seconds.\n', ...
        ltspice_t6_pk_undershoot_ideal_6);
fprintf('        %% diff = %+8.4f (%%).\n', ...
        diff_ideal_t6_pk_undershoot_6);

```

The % difference between MATLAB and LTSpice at the peaks:

```

MATLAB V5 p.o. =      +1.0898 Volts.
LTSpice V5 p.o. =      +1.0900 Volts.
    % diff =  +0.0155 (%).
MATLAB V5 p.u. =      +0.9919 Volts.
LTSpice V5 p.u. =      +0.9918 Volts.
    % diff =  -0.0126 (%).
MATLAB  t p.o. = +2.4092e-04 seconds.
LTSpice t p.o. = +2.3978e-04 seconds.
    % diff =  -0.4726 (%).
MATLAB  t p.u. = +4.8049e-04 seconds.
LTSpice t p.u. = +4.7955e-04 seconds.
    % diff =  -0.1947 (%).

```

Program execution complete

```

disp(' ');
disp('Program execution complete....');

```

Program execution complete....

MATLAB code listing

Published with MATLAB® R2020a