

---

# ELEN 100L (Electric Circuits II): Project 1, Christian Garcia and Logan Barnes

## Table of Contents

Initialize MATLAB Environment .....	1
Setup global variables .....	1
Problem 3 .....	2
Problem 4 .....	8
Problem 5 .....	8

### To Submit:

1. Scanned copy of ALL hand calculations.
2. A MATLAB script and publish the solution using MATLAB's **publish** feature.%
3. Turn in all MATLAB files.
4. Turn in all LTSpice files.
5. Turn in Screenshot of LTSpice measurement.

## Initialize MATLAB Environment

```
clear; clc; clf; cla; close all;
format long; format compact;
```

## Setup global variables

```
% These Ideal Design element values are fixed in the circuit.
VG = 1; % Generator voltage
R1_ideal = 1250 ; % Ohms
R2_ideal = 1333 ; % Ohms
C1_ideal = 0.1e-6 ; % Farads
C2_ideal = 0.1e-6 ; % Farads

% These Actual Design element values are fixed in the circuit.
R1_actual = 1300 ; % Ohms
R2_actual = 1300 ; % Ohms
C1_actual = 0.1e-6 ; % Farads
C2_actual = 0.1e-6 ; % Farads

% Setup values for the poles.
w0 = 3000 ; % Radians/Second
w1 = 20000 ; % Radians/Second
f0 = w0/(2*pi) ; % Hertz
```

```
f1 =      w1/(2*pi)      ;      % Hertz

% Build an array for the angular frequency and convert it to Hertz.
dw = 10;      % Step size for analysis
w = [1:dw:w0-dw, ...
     w0, ...
     w0+dw:dw:w1-dw, ...
     w1, ...
     w1+dw:dw:1.0e6];      % Radians/Second (ensure poles are
                             included)

f =      w/(2*pi)      ;      % Hertz

% These values are used for plotting purposes.
fignum = 1;
plot_left   = 1;      plot_right = 2e5;      % x-axis range (Hertz)
plot_bottom = -90;     plot_top    = 5;      % y-axis range (dB)
```

## Problem 3

```
% Display the component values for the Ideal and Actual designs.
%
```

```
disp(' ');
disp('The Ideal Design component values are:');
fprintf('      R1 = %+11.4f Ohms.\n', R1_ideal );
fprintf('      R2 = %+11.4f Ohms.\n', R2_ideal );
fprintf('      C1 = %+11.4e Farads.\n', C1_ideal );
fprintf('      C2 = %+11.4e Farads.\n', C2_ideal );

disp(' ');
disp('The Actual Design component values are:');
fprintf('      R1 = %+11.4f Ohms.\n', R1_actual );
fprintf('      R2 = %+11.4f Ohms.\n', R2_actual );
fprintf('      C1 = %+11.4e Farads.\n', C1_actual );
fprintf('      C2 = %+11.4e Farads.\n', C2_actual );
```

*The Ideal Design component values are:*

```
R1 = +1250.0000 Ohms.
R2 = +1333.0000 Ohms.
C1 = +1.0000e-07 Farads.
C2 = +1.0000e-07 Farads.
```

*The Actual Design component values are:*

```
R1 = +1300.0000 Ohms.
R2 = +1300.0000 Ohms.
C1 = +1.0000e-07 Farads.
C2 = +1.0000e-07 Farads.
```

Compute the percent differences between the Ideal and Actual design component values.

```
diff_R1_ideal_actual = ( R1_actual - R1_ideal )/abs(R1_ideal)*100;
```

```
diff_R2_ideal_actual = ( R2_actual - R2_ideal )/abs(R2_ideal)*100;
diff_C1_ideal_actual = ( C1_actual - C1_ideal )/abs(C1_ideal)*100;
diff_C2_ideal_actual = ( C2_actual - C2_ideal )/abs(C2_ideal)*100;

disp(' ');
disp('The percent difference between Ideal and Actual design');
disp('component values:');
fprintf('    %% diff R1 = %+8.4f (%%).\n', diff_R1_ideal_actual );
fprintf('    %% diff R2 = %+8.4f (%%).\n', diff_R2_ideal_actual );
fprintf('    %% diff C1 = %+8.4f (%%).\n', diff_C1_ideal_actual );
fprintf('    %% diff C2 = %+8.4f (%%).\n', diff_C2_ideal_actual );
```

*The percent difference between Ideal and Actual design  
component values:*

```
% diff R1 = +4.0000 (%).
% diff R2 = -2.4756 (%).
% diff C1 = +0.0000 (%).
% diff C2 = +0.0000 (%).
```

Display the poles for the target circuit design transfer function.

```
disp(' ');
disp('The poles for the circuit are:');
fprintf('    w0 = %+11.4f Radians/Second.\n',w0);
fprintf('    w1 = %+11.4f Radians/Second.\n',w1);
fprintf('    f0 = %+11.4f Hertz.\n',f0);
fprintf('    f1 = %+11.4f Hertz.\n',f1);
```

*The poles for the circuit are:*

```
w0 = +3000.0000 Radians/Second.
w1 = +20000.0000 Radians/Second.
f0 = +477.4648 Hertz.
f1 = +3183.0989 Hertz.
```

Setup the matrices used to generate the Bode plots for the Ideal and Actual designs.

```
G1_ideal = [ ...
            (1)                (0)                (0); ...
            (-1/R1_ideal)  (1/R1_ideal + 1/R2_ideal)  (-1/R2_ideal); ...
            (0)                (-1/R2_ideal)        (1/R2_ideal)];

G3_ideal = [ 0,0,0;0,0,0;0,0,0 ];

G2_ideal = [ 0,0,0;0,C1_ideal,0;0,0,C2_ideal ];

G1_actual = [ ...
            (1)                (0)                (0); ...
            (-1/R1_actual)  (1/R1_actual + 1/R2_actual)  (-1/
R2_actual); ...
            (0)                (-1/R2_actual)        (1/R2_actual) ];

G3_actual = [ 0,0,0;0,0,0;0,0,0 ];
```

```
G2_actual = [ 0,0,0;0,C1_actual,0;0,0,C2_actual ];
```

```
B = [ 1;0;0 ];
```

Locate the poles in the frequency vector for plotting purposes.

```
% Find the pole values.
pole_1 = 0;
for iter = 1:length(f)           % Locate the first pole
    if (f(iter) == f0)
        pole_1 = iter;
        break;
    end
end

pole_2 = 0;
for iter = pole_1+1:length(f)    % Locate the second pole
    if (f(iter) == f1)
        pole_2 = iter;
        break;
    end
end
```

Calculate the frequency response for the Ideal and Actual designs.

```
Hw_ideal = proj1E100_freqresp( G1_ideal,G2_ideal,G3_ideal,B,w,VG );
Hw_actual = proj1E100_freqresp( G1_actual,G2_actual,G3_actual,B,w,VG );
```

```
% Capture the values at the poles.
```

```
Hw_ideal_f0 = Hw_ideal(pole_1);
Hw_ideal_f1 = Hw_ideal(pole_2);
```


```
Hw_actual_f0 = Hw_actual(pole_1);
Hw_actual_f1 = Hw_actual(pole_2);
```

Generate the plot for  $H_{ideal}(f)$  and indicate where the two poles occur.

```
fignum = fignum+1; figObj = figure(fignum); % Establish a figure
number
set(fignum, 'Name', ['H(f) Ideal Design']); % Name the figure

Hw_ideal_Plot = semilogx( f, Hw_ideal, '-r' ); % Generate plot
grid on; % Turn grid on
xlabel('Frequency (Hz)'); % Label the x-axis
ylabel('Amplitude (dB)'); % Label the y-axis
axis([plot_left, plot_right, ...
      plot_bottom, plot_top]); % Bound plot
title(['Figure ', num2str(fignum, '%-2.u'), ...
      ': H_ideal(f)']);
legend('H_ideal(f)', 'Location', 'NorthEast');

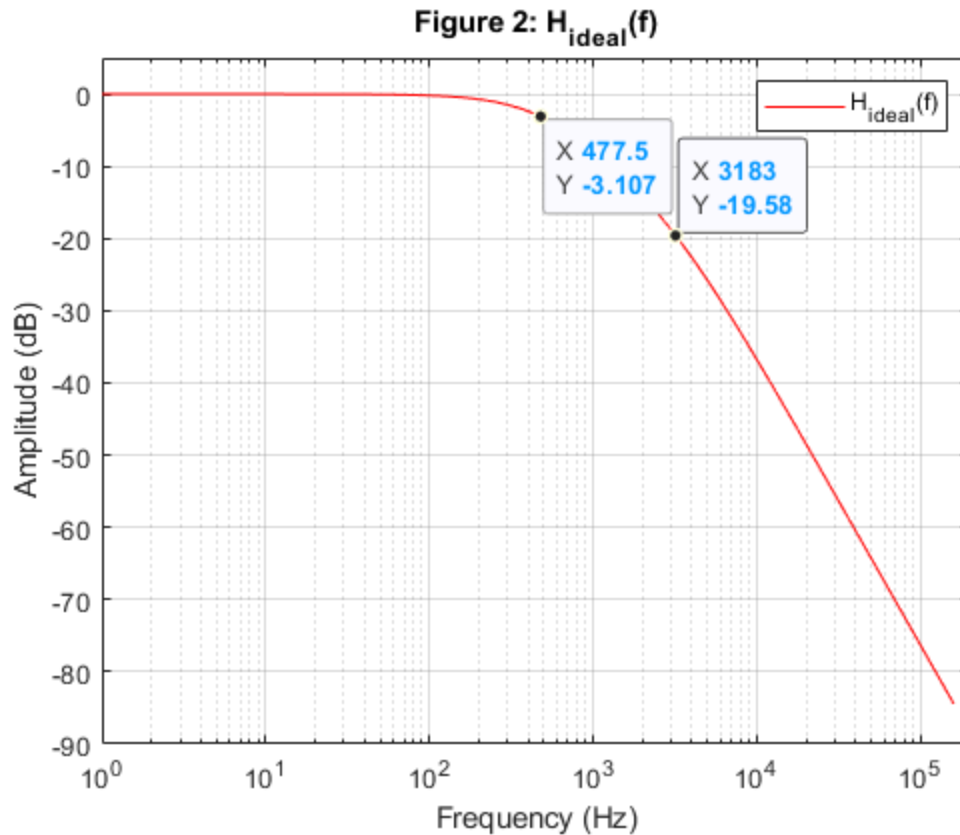% Add cursors to the plot.
makedatatip(Hw_ideal_Plot, [pole_1; pole_2]);
```




Generate the plot for  $H_{actual}(f)$  and indicate where the two poles occur.

```
fignum = fignum+1; figObj = figure(fignum); % Establish a figure
number
set(fignum, 'Name', ['H(f) Actual Design']); % Name the figure

Hw_actual_Plot = semilogx( f , Hw_actual , '-b' ); % Generate
plot
grid on; % Turn grid on
xlabel('Frequency (Hz)'); % Label the x-axis
ylabel('Amplitude (dB)'); % Label the y-axis
axis([plot_left, plot_right, ...
      plot_bottom, plot_top]); % Bound plot
title(['Figure ', num2str(fignum, '%-2.u'), ...
      ': H_a_c_t_u_a_l(f)']);
legend('H_a_c_t_u_a_l(f)', 'Location', 'NorthEast');

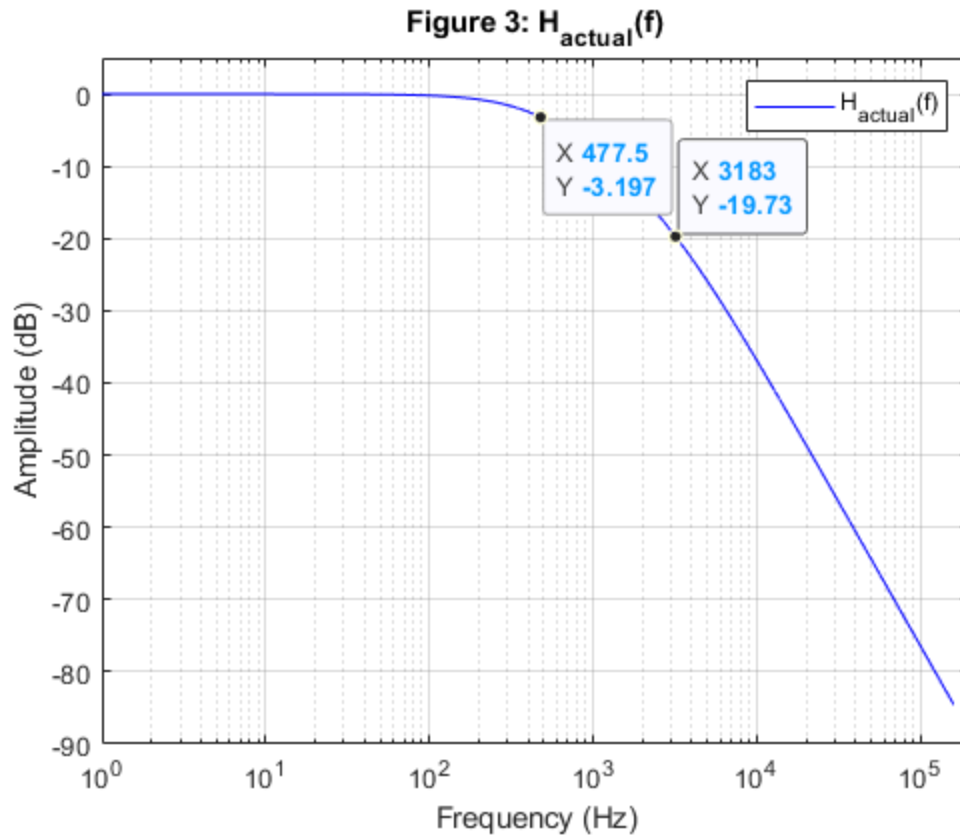% Add cursors to the plot.
makedatatip(Hw_actual_Plot, [pole_1; pole_2]);
```




Generate the plot for comparing  $H_{\text{ideal}}(f)$  and  $H_{\text{actual}}(f)$ .

```

fignum = fignum+1; figObj = figure(fignum); % Establish a figure
number
set(fignum, 'Name', ...
    ['H(f) Ideal and Actual Design']); % Name the figure

Hw_ideal_actual_Plot = ...
    semilogx( f , Hw_ideal , '-r', ...
              f , Hw_actual , '-b'); % Generate

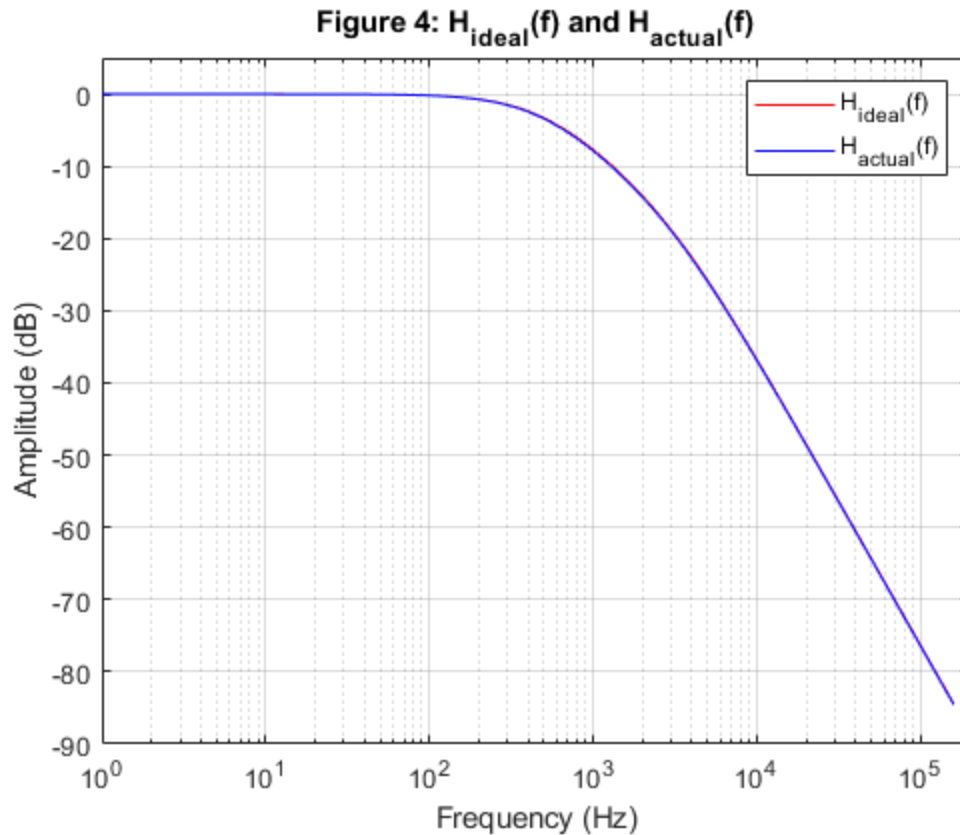plot
grid on; % Turn grid on
xlabel('Frequency (Hz)'); % Label the x-axis
ylabel('Amplitude (dB)'); % Label the y-axis
axis([plot_left, plot_right, ...
      plot_bottom, plot_top]); % Bound plot
title(['Figure ', num2str(fignum, '%-2.u'), ...
      ': H_i_d_e_a_l(f) and H_a_c_t_u_a_l(f)']);
legend('H_i_d_e_a_l(f)', 'H_a_c_t_u_a_l(f)', 'Location', 'NorthEast');
```



Calculate the percent difference between  $H_{ideal}(f)$  and  $H_{actual}(f)$  at the two poles.

```
diff_0_ideal_actual = ( Hw_actual_f0 - Hw_ideal_f0 ) /
abs(Hw_ideal_f0)*100;
diff_1_ideal_actual = ( Hw_actual_f1 - Hw_ideal_f1 ) /
abs(Hw_ideal_f1)*100;

disp(' ');
disp('The difference between Ideal and Actual designs at the poles:');
fprintf('    Ideal Design H( +10.4f ) = %8.4f (dB).\n', f0,
    Hw_ideal_f0);
fprintf('    Actual Design H( +10.4f ) = %8.4f (dB).\n', f0,
    Hw_actual_f0);
fprintf('    %% diff = %8.4f (%%).\n', diff_0_ideal_actual);
fprintf('    Ideal Design H( +10.4f ) = %8.4f (dB).\n', f1,
    Hw_ideal_f1 );
fprintf('    Actual Design H( +10.4f ) = %8.4f (dB).\n', f1,
    Hw_actual_f1 );
fprintf('    %% diff = %8.4f (%%).\n', diff_1_ideal_actual );
```

*The difference between Ideal and Actual designs at the poles:*

```
    Ideal Design H( +477.4648 ) = -3.1066 (dB).
    Actual Design H( +477.4648 ) = -3.1970 (dB).
    % diff = -2.9093 (%).
    Ideal Design H( +3183.0989 ) = -19.5837 (dB).
```

```
Actual Design  $H(+3183.0989) = -19.7321$  (dB).  
% diff = -0.7576 (%).
```

## Problem 4

```
% Calculate the percent difference between  $H_{\text{actual}}(f)$   
(f)}$  
% and  $H_{\text{LTSpice}}(f)$ $ actual designs at the two poles.  
  
Hw_ltspice_f0 = -3.167 ; % dB  
Hw_ltspice_f1 = -19.73 ; % dB  
f0_ltspice = 3000/(2*pi) ; % Hertz  
f1_ltspice = 20000/(2*pi) ; % Hertz  
  
diff_0_actual_ltspice = ( Hw_ideal_f0 - Hw_actual_f0 )/  
abs(Hw_actual_f0)*100;  
diff_1_actual_ltspice = ( Hw_ideal_f1 - Hw_actual_f1 )/  
abs(Hw_actual_f1)*100;  
  
disp(' ');  
disp('The percent difference between MATLAB and LTSpice Actual');  
disp('designs at the poles:');  
fprintf(' Actual MATLAB  $H(+10.4f) = +8.4f$  (dB).\n', ...  
f0, Hw_actual_f0 );  
fprintf(' Actual LTSpice  $H(+10.4f) = +8.4f$  (dB).\n', ...  
f0_ltspice, Hw_ltspice_f0);  
fprintf(' % diff = +8.4f (%) \n', diff_0_actual_ltspice);  
fprintf(' Actual MATLAB  $H(+10.4f) = +8.4f$  (dB).\n', ...  
f1, Hw_actual_f1 );  
fprintf(' Actual LTSpice  $H(+10.4f) = +8.4f$  (dB).\n', ...  
f1_ltspice, Hw_ltspice_f1 );  
fprintf(' % diff = +8.4f (%) \n', diff_1_actual_ltspice );  
  
The percent difference between MATLAB and LTSpice Actual  
designs at the poles:  
Actual MATLAB  $H(+477.4648) = -3.1970$  (dB).  
Actual LTSpice  $H(+477.4648) = -3.1670$  (dB).  
% diff = +2.8271 (%).  
Actual MATLAB  $H(+3183.0989) = -19.7321$  (dB).  
Actual LTSpice  $H(+3183.0989) = -19.7300$  (dB).  
% diff = +0.7519 (%).
```

## Problem 5

Vary the Actual design component values and calculate the frequency response for each variation.

```
% Declare the number of component value iterations.  
value_sets = 5 ;  
  
% Build the actual component vector  
Q_actual = [R1_actual, R2_actual, C1_actual, C2_actual];
```




```
% Generate the frequency response values for the specified number of
% iterations.
[Hw_actual_varied, Q_actual_varied] = ...
    proj1E100_freqresp_varied( Q_actual,B,w,VG,value_sets );

% Capture the values at the poles.
Hw_actual_varied_f0 = zeros(1,value_sets);
Hw_actual_varied_f1 = zeros(1,value_sets);
for iter = 1:value_sets
    Hw_actual_varied_f0(iter) = Hw_actual_varied(iter, pole_1);
    Hw_actual_varied_f1(iter) = Hw_actual_varied(iter, pole_2);
end
```

Generate the plot for variations in the Actual design component values and display all  $H_{varied}(f)$  curves on a single plot.

```
fignum = fignum+1; figObj = figure(fignum); % Establish a figure
number
set(fignum, 'Name', ...
    ['H(f) Actual Design Varied']); % Name the figure

Hw_actual_varied_Plot = ...
    semilogx( f , Hw_actual_varied ); % Generate plot
grid on; % Turn grid on
xlabel('Frequency (Hz)'); % Label the x-axis
ylabel('Amplitude (dB)'); % Label the y-axis
axis([plot_left, plot_right, ...
    plot_bottom, plot_top]); % Bound plot
title(['Figure ', num2str(fignum, '%-2.u'), ...
    ': Varied H_a_c_t_u_a_l(f)']);
legend('H_1(f)', 'H_2(f)', 'H_3(f)', 'H_4(f)', 'H_5(f)', ...
    'Location', 'NorthEast');
```

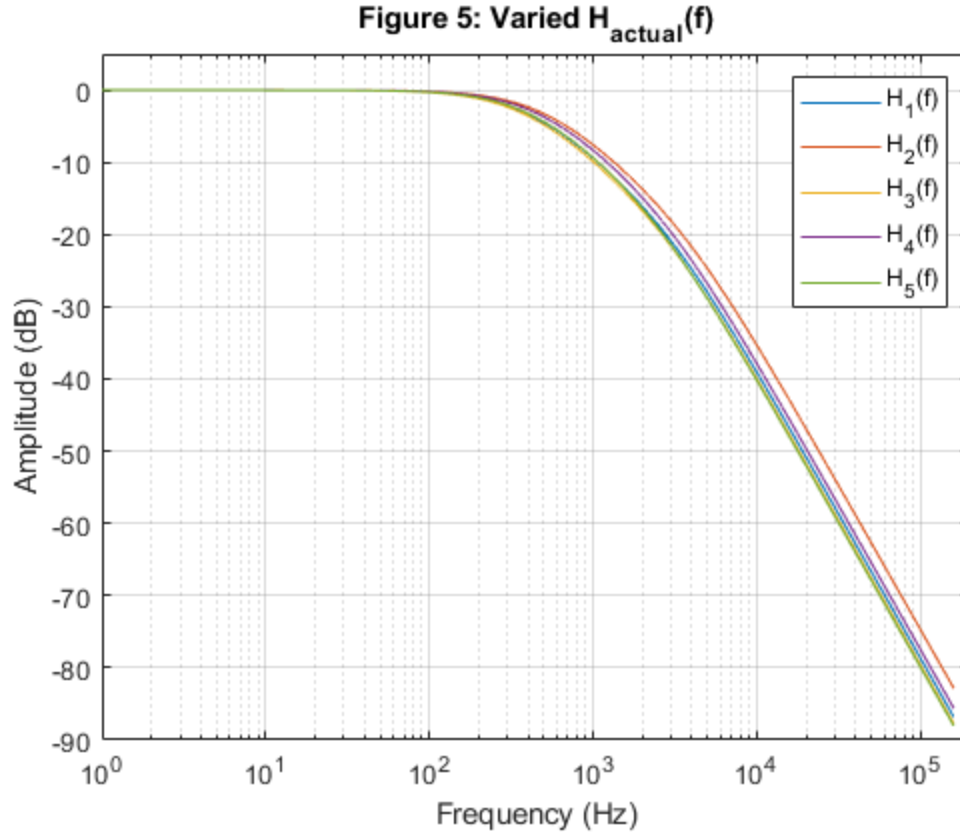

Calculate the percent difference between  $H_{varied}(f)$  and  $H_{actual}(f)$  at the two poles of each variation.

```
diff_0_actual_varied = ...
    (Hw_actual_varied_f0-Hw_actual_f0)/abs(Hw_actual_f0)*100;
diff_1_actual_varied = ...
    ( Hw_actual_varied_f1-Hw_actual_f1 )/abs( Hw_actual_f1 )*100;

disp(' ');
disp('The difference between Varied and Actual designs at the
poles:');
for iter = 1:value_sets
    diff_R1_actual_varied = ...
        (Q_actual_varied(iter,1)-R1_actual)/abs(R1_actual)*100;
    diff_R2_actual_varied = ...
        (Q_actual_varied(iter,2)- R2_actual )/abs( R2_actual )*100;
    diff_C1_actual_varied = ...
        (Q_actual_varied(iter,3)- C1_actual )/abs( C1_actual )*100;
    diff_C2_actual_varied = ...
        (Q_actual_varied(iter,4)-C2_actual)/abs( C2_actual )*100;

    fprintf('    Variation Component Set %-2.u: \n', iter);
    fprintf('        R1 = %+11.4f Ohms,    %% diff = %+8.4f (%%).
\n', ...
        Q_actual_varied(iter,1), diff_R1_actual_varied);
    fprintf('        R2 = %+11.4f Ohms,    %% diff = %+8.4f (%%).
\n', ...
```

```
Q_actual_varied(iter,2), diff_R2_actual_varied );
fprintf('          C1 = %+11.4e Farads,  %% diff = %+8.4f (%%).
\n', ...
        Q_actual_varied(iter,3), diff_C1_actual_varied);
fprintf('          C2 = %+11.4e Farads,  %% diff = %+8.4f (%%).
\n', ...
        Q_actual_varied(iter,4), diff_C2_actual_varied );
fprintf('          Varied Design H(%+10.4f) = %+8.4f (dB).
\n', ...
        f0, Hw_actual_varied_f0(iter));
fprintf('          Actual Design H(%+10.4f) = %+8.4f (dB).
\n', ...
        f0, Hw_actual_f0);
fprintf('          %% diff = %+8.4f (%%).\n', ...
        diff_0_actual_varied(iter));
fprintf('          Varied Design H(%+10.4f) = %+8.4f (dB).
\n', ...
        f1 , Hw_actual_varied_f1(iter) );
fprintf('          Actual Design H(%+10.4f) = %+8.4f (dB).
\n', ...
        f1 , Hw_actual_f1 );
fprintf('          %% diff = %+8.4f (%%).\n', ...
        diff_1_actual_varied(iter) );
end
```

*The difference between Varied and Actual designs at the poles:*

Variation Component Set 1 :

```
R1 = +1463.6563 Ohms,    % diff = +12.5889 (%).
R2 = +1511.0118 Ohms,    % diff = +16.2317 (%).
C1 = +8.5079e-08 Farads, % diff = -14.9205 (%).
C2 = +1.1654e-07 Farads, % diff = +16.5350 (%).
Varied Design H( +477.4648) = -4.2199 (dB).
Actual Design H( +477.4648) = -3.1970 (dB).
% diff = -31.9973 (%).
Varied Design H(+3183.0989) = -21.7375 (dB).
Actual Design H(+3183.0989) = -19.7321 (dB).
% diff = -10.1630 (%).
```

Variation Component Set 2 :

```
R1 = +1368.8268 Ohms,    % diff = +5.2944 (%).
R2 = +1090.7210 Ohms,    % diff = -16.0984 (%).
C1 = +9.1140e-08 Farads, % diff = -8.8601 (%).
C2 = +1.0188e-07 Farads, % diff = +1.8753 (%).
Varied Design H( +477.4648) = -3.0832 (dB).
Actual Design H( +477.4648) = -3.1970 (dB).
% diff = +3.5594 (%).
Varied Design H(+3183.0989) = -18.8651 (dB).
Actual Design H(+3183.0989) = -19.7321 (dB).
% diff = +4.3938 (%).
```

Variation Component Set 3 :

```
R1 = +1537.9036 Ohms,    % diff = +18.3003 (%).
R2 = +1541.7420 Ohms,    % diff = +18.5955 (%).
C1 = +8.6305e-08 Farads, % diff = -13.6955 (%).
C2 = +1.1882e-07 Farads, % diff = +18.8237 (%).
```

Varied Design  $H(+477.4648) = -4.5457$  (dB).  
Actual Design  $H(+477.4648) = -3.1970$  (dB).  
% diff = -42.1883 (%).  
Varied Design  $H(+3183.0989) = -22.4455$  (dB).  
Actual Design  $H(+3183.0989) = -19.7321$  (dB).  
% diff = -13.7512 (%).

Variation Component Set 4 :

$R1 = +1537.7268$  Ohms, % diff = +18.2867 (%).  
 $R2 = +1292.3953$  Ohms, % diff = -0.5850 (%).  
 $C1 = +1.1201e-07$  Farads, % diff = +12.0112 (%).  
 $C2 = +8.5675e-08$  Farads, % diff = -14.3245 (%).  
Varied Design  $H(+477.4648) = -3.4910$  (dB).  
Actual Design  $H(+477.4648) = -3.1970$  (dB).  
% diff = -9.1961 (%).  
Varied Design  $H(+3183.0989) = -20.5206$  (dB).  
Actual Design  $H(+3183.0989) = -19.7321$  (dB).  
% diff = -3.9961 (%).

Variation Component Set 5 :

$R1 = +1259.3159$  Ohms, % diff = -3.1295 (%).  
 $R2 = +1516.1825$  Ohms, % diff = +16.6294 (%).  
 $C1 = +1.1169e-07$  Farads, % diff = +11.6883 (%).  
 $C2 = +1.1838e-07$  Farads, % diff = +18.3797 (%).  
Varied Design  $H(+477.4648) = -4.1140$  (dB).  
Actual Design  $H(+477.4648) = -3.1970$  (dB).  
% diff = -28.6833 (%).  
Varied Design  $H(+3183.0989) = -22.3258$  (dB).  
Actual Design  $H(+3183.0989) = -19.7321$  (dB).  
% diff = -13.1446 (%).